

Tutorial Series 2
MACHINE STRUCTURE

Exercise 1:

Provide the associated functions (First and Second Canonical Forms) for each Karnaugh map:

1)

	AB	00	01	11	10
C					
0				1	1
1			1	1	

2)

	AB	00	01	11	10
CD					
00			1		1
01	1	1	1	1	1
11	1	1	1	1	1
10			1		1

Exercise 2:

Simplify with Karnaugh Map the logical functions represented by the following tables:

1)

	AB	00	01	11	10
C					
0		1			1
1		1	1		1

2)

	AB	00	01	11	10
CD					
00				1	1
01					
11	1				1
10		1		1	1

3)

	AB	00	01	11	10
CD					
00			1		1
01					
11	1	1			
10					1

4)

	AB	00	01	11	10
CD					
00		1	1	1	1
01		1	1		1
11	1	1	1	1	1
10		1	1	1	1

5)

	AB	00	01	11	10
CD					
00		1		1	1
01		1			1
11					
10		1		1	1

6)

	AB	00	01	11	10
CD					
00		1	1	1	
01		1	1		1
11		1	1		1
10		1	1	1	

Exercise 3:

1- Provide the simplified notation (decimal form) of the following Boolean equations:

$$F_1(X,Y,Z) = X + \bar{X}.\bar{Z}$$

$$F_2(A,B,C) = A.B + A.\bar{B}.C$$

2- Provide the simplified notations (two notations) of **F** associated with the following Karnaugh map:

AB \ CD	00	01	11	10
00		1		
01				
11	1			1
10	1		1	1

Exercise 4: (Logic circuit synthesis)

- 1- Simplify $F(A,B,C,D) = \Sigma(1,2,3,5,6,7,8,10,12,13)$
- 2- Draw the associated circuit.

Exercise 5: (Logic circuit synthesis)

A hot beverage vending machine offers the following possible drinks to customers:

- Short sweetened coffee
- Short unsweetened coffee
- Long-sweetened coffee
- Long unsweetened coffee
- Long sweetened coffee with milk
- Long unsweetened coffee with milk
- Sweetened milk
- Unsweetened milk

The vending machine orders are:

- short coffee = **a**
- long coffee = **b**
- sugar = **s**
- milk = **m**

Question: Provide the synthesis of the associated circuit.

Exercise 6: (Logic circuit synthesis)

Three switches, **S₁**, **S₂**, and **S₃**, control the startup of a system with two motors, **M₁** and **M₂**.

- a- If one or more switches are activated, motor **M₁** starts.
- b- If at least two switches are activated, motor **M₂** starts.

Question: Provide the synthesis of the associated circuit.

Exercise 7:


Let **G** be a Boolean function such that:

$$G = (x.y.z) + (x+y)$$

- 1- Draw the circuit associated with G.
- 2- Use NOT, AND, and OR gates to express G, and draw the associated circuit for G.

Exercise 8: (Analysis of a logic circuit)

Consider the following flowchart:

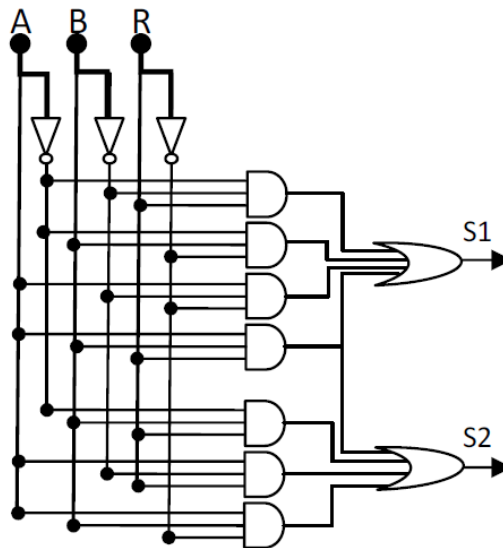

The analysis of this circuit involves answering these questions:

- 1- Determine the functions of the circuit (S_1 and S_2).
- 2- Simplify the equations S_1 and S_2 (using only AND, OR, and NOT).
- 3- Reuse AND, OR, NOT, XOR, and XNOR gates to obtain the equivalent circuit with fewer logic gates.
- 4- Draw the obtained circuit.

Exercise 9:

Provide the logic circuits of a half binary subtractor and a full subtractor.

Exercise 10:

Find the combinational circuit that converts binary (3 bits) to Gray code.